

Tutorial Assignments: Analog Signal Processing (EE60032),

Department of Electrical Engineering, Indian Institute of Technology, Kharagpur

Faculty: Ashis Maity

Session: Autumn 2019

1. Find the resolution for a DAC if the output voltage is desired to change in 1 mV increments while using a reference voltage of 5V. [Ans: 13 bits]
2. From any non-ideal characteristics of the converter, find out INL and DNL. [One example has been shown in the class.]
3. A sinusoidal waveform is applied to a 12 bit ADC and the output is digitally analyzed. If the fundamental has a normalized power of 9 W while the remaining noise power is 0.5  $\mu$ W, what is the effective number of bits of the converter? [Ans: 10.2 bits]
4. An 8-bit ADC has a reference voltage  $V_{ref}=4V$ . Find the RMS value of the quantization noise. Also find SNR of the ADC for full scale sine wave input and half scale sine wave input. [Solved in the class]
5. To a serial charge redistribution DAC, the word 1101 is applied to convert as an analog output. Follow through the sequence of events that result in conversion of this digital input word. [Solved in the class]
6. Assume  $M=2$  and  $K=2$ , find out the transfer characteristic of this DAC if the scaling factor of the LSB sub-DAC is  $3/8$  instead of  $1/4$ . Assume  $V_{ref}=1 V$ . What is the  $\pm INL$  and  $\pm DNL$  for this DAC? Is this DAC monotonic? [Ans:  $INL=1.5LSB$ ,  $DNL=-1.5LSB$ ]

